

Third Semester B.E. Degree Examination, December 2010

Logic Design

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART - A

- Draw the logic circuit whose Boolean equation is $Y = \overline{A + B + C}$, use only NAND gates. (04 Marks)
 - Find the minimal sum and minimal product using Karnaugh map.
 $f(a, b, c, d) = \sum m(6, 7, 9, 10, 13) + d(1, 4, 5, 11)$ (08 Marks)
 - Find the prime implicants for the following function using Quine Mccluskey method:
 $f(a, b, c, d) = \sum m(1, 2, 8, 9, 10, 12, 13, 14)$ (08 Marks)
- Implement the following function using a 8 : 1 multiplexer :
 $f(a, b, c, d) = \sum m(0, 1, 5, 6, 8, 10, 12, 15)$ (05 Marks)
 - Describe the working principle of a 3 : 8 decoder. Realize the following Boolean expressions using the 3 : 8 decoder :
 $F_1(A, B, C) = \sum m(1, 2, 3, 4)$ $F_2(A, B, C) = \sum m(3, 5, 7)$ (06 Marks)
 - What is PLA? How does PLA differ from PAL? (05 Marks)
 - Write HDL code for a 4 to 1 Mux considering any model. (04 Marks)
- How is 2's complement representation used to perform subtraction? Give an example. (04 Marks)
 - Show how two 7483 can be used to add/subtract two 8 bit numbers. Draw a neat diagram and explain its working. (08 Marks)
 - Design a 2 bit fast adder. Give its implementation using gates. (08 Marks)
- Calculate the clock cycle time for a system that uses a clock, that has a frequency of :
 i) 10 MHz ii) 6 MHz iii) 750 KHz (03 Marks)
 - With a neat block diagram, explain the working of a Master-Slave JK flip flop. Also write its truth table. (07 Marks)
 - Explain the function of the circuit shown here with the state transition diagram. (10 Marks)


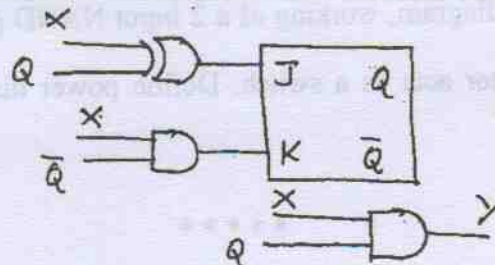


Fig.Q4(c)


PART - B

- 5 a. Draw the logic diagram of a 4 bit serial in serial out shift register using JK flip flop and explain its working with an example. (05 Marks)
- b. Give the HDL code for a shift register of 5 bits constructed using D flip flops. (03 Marks)
- c. Construct a mod 8 asynchronous counter and write the truth table and draw waveforms. (06 Marks)
- d. Design a mod 4 synchronous counter using a -ve edge triggered JK flip flop. Draw the state transition diagram. (06 Marks)

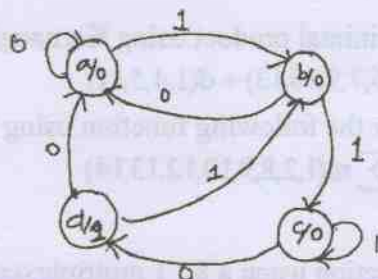- 6 a. For the following state transition diagram, design equations for Moore model and generate the circuit diagram. (10 Marks)



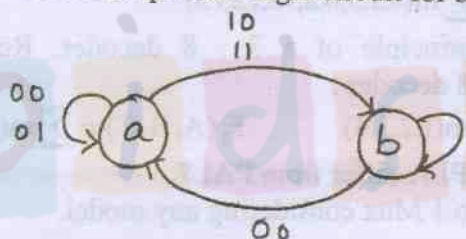- b. Design an asynchronous sequential logic circuit for state transition diagram shown below:



- c. How does state transition diagram of a Moore machine differ from Mealy machine? (06 Marks)

- 7 a. Draw a binary ladder network for a digital input 1000 and obtain its equivalent circuit. (06 Marks)
- b. Explain the concept of "successive approximation" of a A/D converter. (08 Marks)
- c. In a 8 bit counter type A/D converter driven by 500 KHz clock, find : (06 Marks)
 - i) Conversion time
 - ii) Average conversion time
 - iii) Maximum conversion time.

- 8 a. Explain the working of CMOS NAND, NOR gates. (08 Marks)
- b. Explain with a neat diagram, working of a 2 input NAND gate TTL with totempole output. (07 Marks)
- c. Explain how transistor acts as a switch. Define power dissipation and propagation delay time. (05 Marks)

