

- 3 a. Choose the correct answers for the following : (04 Mark)
- The intersection of a dc load line and the output characteristics of a transistor is called
 - Q – point
 - Quiescent point
 - Operating point
 - All of these
 - For an emitter follower, the voltage gain is
 - unity
 - greater than unity
 - less than unity
 - zero
 - The best biasing stability is achieved by using _____ biasing circuit.
 - fixed
 - collector to base
 - voltage divider
 - None of these
 - In self bias or emitter bias circuit _____ is connected between emitter and ground
 - inductor
 - capacitor
 - resistor
 - transformer
- b. Explain the concepts of base bias techniques using NPN transistor. (10 Marks)
- c. Calculate the Q – point values for the circuit of collector to base circuit. Given $R_B = 100 \text{ K}\Omega$, $R_C = 10 \text{ K}\Omega$, $V_{CC} = 12 \text{ V}$ and $\beta_{dc} = 100$. (06 Marks)
- 4 a. Choose the correct answers for the following : (04 Marks)
- A SCR has _____ number of layers
 - one
 - two
 - three
 - Four
 - The minimum point in VI characteristic of UJT is known as _____ point
 - negative
 - valley
 - latching
 - conducting
 - The FET is a _____ controlled device
 - current
 - voltage
 - power
 - None of these
 - The relaxation oscillator uses
 - MOSFET
 - SCR
 - BJT
 - UJT.
- b. Draw two transistor equivalent circuit of SCR. Also plot V – I characteristics and explain various regions of operations. (10 Marks)
- c. Explain with suitable diagram and waveforms, how UJT can be used as a relaxation oscillator. (06 Marks)

PART – B

- 5 a. Choose the correct answers for the following : (04 Marks)
- Oscillator uses _____ type of feedback
 - positive
 - negative
 - both
 - None of these
 - A phase shift oscillator has
 - three RC circuits
 - three LC circuits
 - a T - type circuit
 - a π type circuit
 - The frequency of Hartley oscillator is $f =$ _____
 - $\frac{1}{2\pi\sqrt{LC}}$
 - $\frac{1}{2\pi\sqrt{RC}}$
 - $\frac{1}{2\pi\sqrt{C}}$
 - $\frac{1}{2\pi LC}$
 - The upper and lower critical frequencies are sometimes called the
 - power frequencies
 - half power frequencies
 - 6 dB points
 - None of these
- b. Explain with a neat diagram, the working of single stage RC coupled amplifiers with its frequency response. (08 Marks)
- c. Give any four advantages of negative feedback in amplifier. (04 Marks)
- d. In a colpitts oscillator, if the desired frequency is 800 KHz, determine the values of L and C_{eq} if $C_1 = C_2 = 10 \text{ picofarad}$. (04 Marks)

- 6 a. Choose the correct answers for the following : (04 Marks)
- The CMRR is given by ____
 A) $A_d \times A_c$ B) A_c / A_d C) A_d / A_c D) $20 \log A_c / A_d$
 - The gain of the inverting amplifier using $R_f = 10 \text{ K}\Omega$ and $R_1 = 1 \text{ K}\Omega$ is ____
 A) -10 B) -11 C) 10 D) 11
 - The gain of the voltage follower is ____
 A) zero B) infinite. C) negative D) unity
 - The screen of CRT is coated with ____
 A) chromium B) phosphor C) carbon D) germanium
- b. Calculate the output voltage of a three input summing amplifier : Given $R_1 = 200 \text{ K}\Omega$, $R_2 = 250 \text{ K}\Omega$, $R_3 = 500 \text{ K}\Omega$ and $R_f = 1 \text{ M}\Omega$, $V_1 = -2\text{V}$, $V_2 = 2\text{V}$ and $V_3 = 1 \text{ V}$. (06 Marks)
- c. Show, how an op amp can be used as an integrator. Derive an expression for output voltage. (06 Marks)
- d. Give any four applications of CRO. (04 Marks)
- 7 a. Choose the correct answers for the following : (04 Marks)
- The modulating frequency is ____ carrier frequency
 A) lower than B) higher than C) equal to D) None of these
 - The modulation is done in ____
 A) transmitter B) receiver
 C) none of the above D) between transmitter and receiver.
 - The 2's complement of 1010 gives
 A) 1111 B) 0110 C) 0010 D) 0101
 - In binary numbers, shifting the binary point one place to right
 A) divides by 2 B) decreases by 10
 C) increases by 10 D) multiplies by 2
- b. With suitable block diagram, explain the function of superheterodyne receiver. (08 Marks)
- c. Convert $(ABCD)_{16} = ()_2 = ()_8 = ()_{10} = ()_{\text{BCD}}$. (04 Marks)
- d. Subtract : $(28)_{10} - (19)_{10}$ using both 1's complement and 2's complement methods. (04 Marks)
- 8 a. Choose the correct answers for the following : (04 Marks)
- When demorganis theorem applied to $(A + B)$, we get ____
 A) $A + B$ B) $\bar{A} \bar{B}$ C) A D) B
 - $Y = \bar{A}B + \bar{B}A$ is a Boolean expression for ____
 A) EX - OR B) EX - NAND
 C) EX - NOR D) none of these
 - The example for universal gate is ____
 A) NOT B) NOR C) OR D) AND
 - The expression for half adder carry 'C' with inputs 'A' and 'B' is given by
 A) $A + B$ B) AB C) $\bar{A} \bar{B}$ D) none of these
- b. i) Realize the NAND gate using minimum number of NOR gates
 ii) Simplify $M = XYZ + X\bar{Y}Z + \bar{Z}XY$ and realize using of NOR gates. (08 Marks)
- c. Realize a full adder using two half adders and an OR gate with truth table. (08 Marks)